

# Laboratorio di Elettronica Digitale

## - PAL: Programmable Array Logic -



Programmazione a livello  
basso => si programmano le  
porte logiche

vanno su applicazioni che  
costano (civile o militare che  
sia)

## ➤ How logic circuits can be used ?




Circuits exist(ed) that integrates simple logic functions

Es. SN 7400 with 4 NAND gates

  

With this solution a simple clock needs a full board!

   - In modern circuits all the logics are integrated in a single, programmable chip: a **Programmable Logic Device (PLD)**





- A single PLD can easily integrate ~ **500.000 gates** with 500-1000 pins !
- Let's try and understand how to use it ...


## - Open Drain / Open Collector Gates -

Open Drain **NOT CMOS**

Open Collector NOT TTL

  


 Open drain/collector gates are labelled with a star or similar symbol




- The «open drain gates are obtained by removing the «high» MOS in CMOS and the «high» transistor-resistor-diode in TTL.
- The gate can only drive low, i.e. sink current from the output to ground, but can't source current from power to the output.
- Note: A Open Drain CMOS NOT gate can be realized with a single NMOS transistor

## - Open Drain / Open Collector Gates -

 

- The gate needs a pull-up to drive the high level
- When Out = '0' the gate shorts the output to ground => 0V in Out
- When Out = '1' the gate is disconnected => Out = Vcc thanks to the pull-up

## - Open Drain / Open Collector Gates -

 


- The output of several gates can be connected on the same bus without risk of bus contention and circuit damage<sup>1</sup>
- In fact, each output or sinks current or is disconnected. The current is sourced to the bus only through the resistor R. => No risk of short

<sup>1</sup>see Elettronica dei Sistemi Digitali course


 
## - Wired Logic -


- Open Drain/Collector gates can be used for wired logic



Out is HIGH only if ALL of the N In are LOW (Output disconnected). When one or more In is high, the corresponding output sinks current to ground and the Out goes LOW. This is a NOR gate with N inputs.

NOR



| In <sub>1</sub> | In <sub>2</sub> | ... | In <sub>N</sub> | Out |
|-----------------|-----------------|-----|-----------------|-----|
| 0               | 0               | ... | 0               | 1   |
| 0               | 0               | ... | 1               | 0   |
| 0               | 1               | ... | 0               | 0   |
| 0               | 1               | ... | 1               | 0   |
| 1               | 0               | ... | 0               | 0   |
| 1               | 0               | ... | 1               | 0   |
| 1               | 1               | ... | 0               | 0   |
| 1               | 1               | ... | 1               | 0   |

 

- Wired logic represents a simple way of realizing gates with several inputs
  
## - Wired Logic -


➤ If we use a **buffer instead of a NOT** we have a wired AND



AND

| $In_1$ | $In_2$ | ... | $In_N$ | Out |
|--------|--------|-----|--------|-----|
| 0      | 0      | ... | 0      | 0   |
| 0      | 0      | ... | 1      | 0   |
| 0      | 1      | ... | 0      | 0   |
| 0      | 1      | ... | 1      | 0   |
| 1      | 0      | ... | 0      | 0   |
| 1      | 0      | ... | 1      | 0   |
| 1      | 1      | ... | 0      | 0   |
| 1      | 1      | ... | 1      | 1   |

 Out is HIGH only if ALL of the N In are HIGH (Principal Mosfet Off). This is a AND gate with N inputs






## - Programmable Wired Logic -

➤ Towards a programmable logic...

A wired logic can be represented as:

For example wired AND



 


$$\text{Out} = I_1 \cdot I_2 \cdot I_4 \cdot I_6 \cdot I_9$$

The possible inputs are reported as crossing lines. The inputs actually connected are labelled with a cross. Programming the AND means changing the actual connected inputs (crosses) among the possible inputs  $I_{1-10}$

## - Programmable Wired Logic -

➤ For example...

   


How can this programmability be obtained in a real circuit?



## - Programmable Wired Logic -


➤ ...By using matallic fuses

 

A «fuse» is made by a thin metal strip. A high current is used to blow the fuse and remove the connection. Once the connection is removed it can not be restored. These devices **can be programmed once (OTP)**
 
## - Programmable Wired Logic -

➤ ...By using the Floating gate Avalance injection MOS (FAMOS)




The FAMOS is used also in EEPROM and can be re-programmed several times. When electrons are stored in the floating gate, the FAMOS is an open circuit, when electrons are removed from the floating gate, the FAMOS works like a standard MOS.

Note that in this case we use standard input buffers (NOT in this case), since each NOT is connected just to one FAMOS gate

## - Programmable Wired Logic -


### ➤ Programmable NOR with FAMOS

 

Out is HIGH only if ALL of the N In are LOW (FAMOS Off). When one or more In is high, the corresponding FAMOS is switched ON, and the Out goes LOW. This is a NOR gate with N inputs. Of course, disabled FAMOS (with electrons on floating gate) are always OFF and the corresponding input does not matter


NOR

| In <sub>1</sub> | In <sub>2</sub> | ... | In <sub>N</sub> | Out |
|-----------------|-----------------|-----|-----------------|-----|
| 0               | 0               | ... | 0               | 1   |
| 0               | 0               | ... | 1               | 0   |
| 0               | 1               | ... | 0               | 0   |
| 0               | 1               | ... | 1               | 0   |
| 1               | 0               | ... | 0               | 0   |
| 1               | 0               | ... | 1               | 0   |
| 1               | 1               | ... | 0               | 0   |
| 1               | 1               | ... | 1               | 0   |

 

## - Wired Logic -


### ➤ Programmable AND with FAMOS

 

AND


| In <sub>1</sub> | In <sub>2</sub> | ... | In <sub>N</sub> | Out |
|-----------------|-----------------|-----|-----------------|-----|
| 0               | 0               | ... | 0               | 0   |
| 0               | 0               | ... | 1               | 0   |
| 0               | 1               | ... | 0               | 0   |
| 0               | 1               | ... | 1               | 0   |
| 1               | 0               | ... | 0               | 0   |
| 1               | 0               | ... | 1               | 0   |
| 1               | 1               | ... | 0               | 0   |
| 1               | 1               | ... | 1               | 1   |

 If a NOT is used as input buffer, we obtain a programmable AND instead of NOR


 
## - Programmable AND Matrixes-

➤ We can produce a matrix of wired AND as follows




In this example we have a **N input – M output programmable AND** matrix  
The FAMOSes select which inputs are connected to which outputs



## - Programmable AND Matrix-


➤ The matrix is usually represented as :

 

In this example we have 6 wired AND with 10 possible inputs each  
Each cross represents a «working» FAMOS, the missing cross a  
«isolating» FAMOS
 
## - PAL: Programmable Array Logic -


- PLA is realized by a programmable AND matrix and a fixed OR



- The inputs feed the matrix in direct and negate form

## - PAL: Programmable Array Logic -

➤ The PAL is usually represented as :

 

In this example 8 input feed a programmable AND matrix followed by a 6 input OR

## - PAL: Programmable Array Logic -

➤ Every logic function has a AND-OR representation (2-level).




Every logic function can be programmed in a PAL  
( provided that the PAL has enough resources )

Example:

| $I_1$ | $I_2$ | Out |
|-------|-------|-----|
| 0     | 0     | 0   |
| 0     | 1     | 1   |
| 1     | 0     | 1   |
| 1     | 1     | 0   |

 
$$\text{Out} = (\overline{I_1} \cdot I_2) + (I_1 \cdot \overline{I_2})$$



## - PAL: Programmable Array Logic -

Example:

| $I_1$                  | $I_2$ | $I_3$ | $I_4$ | Out |
|------------------------|-------|-------|-------|-----|
| 0                      | 0     | 0     | 0     | 1   |
| 0                      | 1     | 0     | 1     | 1   |
| 1                      | 0     | 0     | 1     | 1   |
| 1                      | 1     | 0     | 0     | 1   |
| 1                      | 1     | 0     | 1     | 1   |
| All other combinations |       |       |       | 0   |

 


$$\text{Out} = (\overline{I_1} \cdot \overline{I_2} \cdot \overline{I_3} \cdot \overline{I_4}) + (\overline{I_1} \cdot I_2 \cdot \overline{I_3} \cdot I_4) + (I_1 \cdot \overline{I_2} \cdot \overline{I_3} \cdot I_4) + (I_1 \cdot I_2 \cdot \overline{I_3} \cdot \overline{I_4}) + (I_1 \cdot I_2 \cdot \overline{I_3} \cdot I_4)$$

Every product term (truth table line) is realized by a wired AND in the PAL

A function with N inputs and M product terms needs a PAL with, at least,  
N inputs and M lines towards the OR
 
## - PAL: Programmable Array Logic -

➤ The PAL includes several output (OR gates)



Example:


| $I_1$ | $I_2$ | Out <sub>1</sub> | Out <sub>2</sub> |
|-------|-------|------------------|------------------|
| 0     | 0     | 0                | 0                |
| 0     | 1     | 1                | 0                |
| 1     | 0     | 1                | 0                |
| 1     | 1     | 0                | 1                |

The **inputs** (matrix columns) **are common to all outputs**

## - PAL: Programmable Array Logic -

Example:


| $I_3$ | $I_2$ | $I_1$ | Out |
|-------|-------|-------|-----|
| 0     | 0     | 0     | 1   |
| 0     | 0     | 1     | 1   |
| 0     | 1     | 0     | 1   |
| 0     | 1     | 1     | 1   |
| 1     | 0     | 0     | 1   |
| 1     | 0     | 1     | 1   |
| 1     | 1     | 0     | 1   |
| 1     | 1     | 1     | 0   |

 

The 'out' of this logic function has seven '1'. As it is, it needs 7 product terms, but this PAL has only 6. This function cannot be realized. However it has only a '0' in output, so  $\overline{\text{Out}} = I_3 \cdot I_2 \cdot I_1$ . The neg function would be very easy to realize....



## - PAL: Improvements: Additional XOR -

 


The XOR is sort of «programmable NOT». If one input is '1' the other is inverted, if it is '0' the other is not inverted. With a FAMOS we can decide if inverting or not the output. This is useful for the synthesis of function with more '1' than '0' in the output



## - PAL: Improvements: Additional XOR -

Example:


| $I_3$ | $I_2$ | $I_1$ | Out | $\overline{\text{Out}}$ |
|-------|-------|-------|-----|-------------------------|
| 0     | 0     | 0     | 1   | 0                       |
| 0     | 0     | 1     | 1   | 0                       |
| 0     | 1     | 0     | 1   | 0                       |
| 0     | 1     | 1     | 1   | 0                       |
| 1     | 0     | 0     | 1   | 0                       |
| 1     | 0     | 1     | 1   | 0                       |
| 1     | 1     | 0     | 1   | 0                       |
| 1     | 1     | 1     | 0   | 1                       |

 

In the AND matrix the  $\overline{\text{Out}}$  is coded, then the final XOR inverts the  $\overline{\text{Out}}$ .

The programmable XOR allows to synthesize the '1s' or the '0s' of a logic function, whichever are more convenient

## - PAL: Improvements: feedback line -

 

It is possible to feed an output back in the AND matrix. This allows the realization of more complex functions

## - PAL: Improvements: feedback line -


Example:

| $I_3$ | $I_2$ | $I_1$ | Out |
|-------|-------|-------|-----|
| 0     | 0     | 0     | 1   |
| 0     | 0     | 1     | 1   |
| 0     | 1     | 0     | 1   |
| 0     | 1     | 1     | 1   |
| 1     | 0     | 0     | 1   |
| 1     | 0     | 1     | 1   |
| 1     | 1     | 0     | 1   |
| 1     | 1     | 1     | 0   |

Out1

Out2
 
$$\text{Out2} = \text{Out1} + I_3 \cdot I_2 \cdot \overline{I_1}$$




Out1 synthesizes the first six '1s' of the table. Out1 is routed back in the AND matrix and added to the last '1'.

This is a 4-level function implementation => more delay

## - PAL: towards commercial devices -

### ➤ Programmable Input/Output (I/O)

 

PIN

#### Legend



-  Output PIN
-  Input PIN
-  I/O PIN

The external connections of a device can be dedicated inputs (e.g.  $I_1 - I_7$ ), dedicated outputs ( $O_1$ ), or programmable Input/Output ( $I/O_1$ ).

When the buffer 3 state is active ( $En = 1$ ) the pin is an output, otherwise ( $En = 0$ ) it is an Input. The  $En$  signal can be programmed from the AND matrix

## - PAL: Programmable Array Logic -


### ➤ Programmable Input/Output (I/O)

  

$I_7 \cdot \overline{I_7} = En = 0$ , thus the buffer is disabled and the PIN is an input, which feeds the AND matrix like the other inputs. In this case the logic connected to the disabled buffer can't be used and is wasted.

## - PAL: Programmable Array Logic -


### ► Programmable Input/Output (I/O)

 

When the AND connected to En has not connections (no crosses) En = '1' (pull-up on the line) and the PIN is an output. Note that the output signal has a feedback into the AND matrix, and can be re-used in the logic

## - PAL: Programmable Array Logic -


### ➤ Programmable Input/Output (I/O)

 


In this example  $En = I_7$  and  $I_7$  works as an output enable.

More complex configurations are possible with a suitable programming

## - Commercial Example: PAL 16L8 -

 

PAL 16L8

 


PAL with

- 10 dedicated input (I)
- 2 dedicated output (O) with 3 states
- 6 pin switchable between I or O (I/O)



## - Registered Programmable Logic -

➤ A flip flop D is added after the OR

 


The clock is fed by a dedicated input to all the flip flops of the devices

## - Registered Programmable Logic -
 
### ➤ Register by-passes

A programmable mux can be added to bypass (or not) the register




The mux can be programmed to select the output from the register (Q) or bypass the register (D).

The cell synthesizes sequential or combinatorial logic, depending on how the mux is programmed.


## - Commercial Example: PAL 16V8 -

PAL 16L8 Cell

 


The behaviour of the cell is programmed by the SL0,SG1,SL1 bits

## - Commercial Example: PAL 16V8 -

 

 The clk is  
common to all of  
the registers




The PAL 16V8 has 8 cells

Other cells below...

## - Commercial Example -

DIE of PAL 16L8

 

cells





AND Matrix

Wire bonding pads



## - Commercial Example -

  


## - Summary -

- Wired logic is useful to obtain logic functions with several inputs
- Fuses or FAMOS allows programmability
- Programmable AND matrix followed by fixed OR allows the realization of programmable 2-level logic functions
- Several improvements (feedback, XOR, etc.) can be added
- A register can be present for sequential logic implementation
- PAL devices are (were) commercially available which implement such functions
 
## - Wired Logic -


➤ If we add an inverter on each input we have a wired AND



AND

| In <sub>1</sub> | In <sub>2</sub> | ... | In <sub>N</sub> | Out |
|-----------------|-----------------|-----|-----------------|-----|
| 0               | 0               | ... | 0               | 0   |
| 0               | 0               | ... | 1               | 0   |
| 0               | 1               | ... | 0               | 0   |
| 0               | 1               | ... | 1               | 0   |
| 1               | 0               | ... | 0               | 0   |
| 1               | 0               | ... | 1               | 0   |
| 1               | 1               | ... | 0               | 0   |
| 1               | 1               | ... | 1               | 1   |

 
Out is HIGH only if ALL of the N In are HIGH (Principal Mosfet Off). This is a AND gate with N inputs




 
## - Open Drain/Collector Gates -

- the cell used in the Wired AND is an «open drain» gate



- The «open drain gates are obtained by removing the «high» MOS from the standard gate. Doing so, the gate can only drive low.
- Open drain gates are labelled with a star or similar symbol



# CPLD Architecture

Prof. Stefano Ricci



UNIVERSITÀ  
DEGLI STUDI  
FIRENZE

**DINFO**  
DIPARTIMENTO DI  
INGEGNERIA  
DELL'INFORMAZIONE

Updated 02/2025

## - CPLD -


- CPLD: Complex Programmable Logic Device
- CPLDs represent the 'natural' development of the PAL  
But with enhanced capacity...

|         | PAL  | CPLD       |
|---------|------|------------|
| I/O pin | ~ 30 | Up to 250  |
| Cells   | ~ 10 | Up to 1700 |


 
## - CPLD architecture -

- CPLD is basically an array of interconnected PALs



alla programmabilità di ciascuna PAL viene aggiunta tutta la parte di interconnessione => posso decidere come interconnettere ingressi uscite di diverse PAL  
=> ho bus di interconnessione configurabili

- The interconnections among PALs are programmable, i.e. the user can select which lines are routed to a specific PAL




## - CPLD architecture -

la configurabilità di questi dispositivi è legata al fgmos (memoria flash) => una volta configurata una cella questa rimane anche per diverso tempo => una volta che lo accendo questo se configurato risponde subito  
viceversa le fpga si basano sulle RAM => all'accensione questa è azzerata e dunque necessità di una fase di caricamento dei dati => "ha bisogno di un po' di tempo per accendersi"  
=> per cui l'utilizzo dei due dispositivi cambia a seconda dei requisiti


- Esempio commerciale: Famiglia MAX3000 di Altera
- Tecnologia 0.3 um
- Basata su memoria Flash

## - MAX 3000 CPLD - Architettura

 
 
## - MAX 3000 CPLD - Macrocella

matrice di and-or (ingressi dal basso)  
con connessioni configurabili (sempre tramite fgmos)




36 fili dal PIA comuni a tutte le macrocelle

## - MAX 3000 CPLD – Shareable Expanders

foto riprese dal datasheet del dispositivo

 
*Shareable expanders can be shared by any or all macrocells in an LAB.*




16 fili => una per macrocella  
=> a questi posso aggiungere un termine prodotto negato  
=> utilizzato come ingresso per le funzioni somma-prodotto



## - MAX 3000 CPLD – Parallel Expander

 


## - MAX 3000 CPLD – I/O Blocks

 
 
## - Timing MAX 3000 CPLD – Timing model

nei cpld c'è da preoccuparsi  
delle temporizzazioni... non è  
come nel caso dei microcontrollori

fare codice per cpld deve tener conto di queste =>  
altrimenti non ho sicurezza di avere codice funzionante e  
affidabile => altrimenti dipende dal caso...



software fa in modo automatico i calcoli per il modello di temporizzazione => usando tutte le info riguardanti i ritardi dei vari componenti

➤ For details and examples see «TimingMax7000.pdf» in moodle

evidenziato il percorso che facciamo nel caso in cui si percorre tutti i passi per cui si vuole riportare in uscita l'ingresso inserito (caso in cui non aggiungo nessuna funzione => ho solo funzione identità)

**Table 17. EPM3032A Internal Timing Parameters (Part 1 of 2)** *Note (1)*

| Symbol     | Parameter                                                                                     | Conditions<br><br>la scelta dei "tratti" dipende dal tipo di CPLD con cui si ha a che fare | Speed Grade |     |     |     |     |     | Unit<br><br>ovviamente i più veloci vanno a prezzi + alti (sono tutte garantite funzionanti) |
|------------|-----------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------|-------------|-----|-----|-----|-----|-----|----------------------------------------------------------------------------------------------|
|            |                                                                                               |                                                                                            | -4          |     | -7  |     | -10 |     |                                                                                              |
|            |                                                                                               |                                                                                            | Min         | Max | Min | Max | Min | Max |                                                                                              |
| $t_{IN}$   | Input pad and buffer delay                                                                    |                                                                                            |             | 0.7 |     | 1.2 |     | 1.5 | ns                                                                                           |
| $t_{IO}$   | I/O input pad and buffer delay                                                                |                                                                                            |             | 0.7 |     | 1.2 |     | 1.5 | ns                                                                                           |
| $t_{SEXP}$ | Shared expander delay                                                                         |                                                                                            |             | 1.9 |     | 3.1 |     | 4.0 | ns                                                                                           |
| $t_{PEXP}$ | Parallel expander delay                                                                       |                                                                                            |             | 0.5 |     | 0.8 |     | 1.0 | ns                                                                                           |
| $t_{LAD}$  | Logic array delay                                                                             |                                                                                            |             | 1.5 |     | 2.5 |     | 3.3 | ns                                                                                           |
| $t_{LAC}$  | Logic control array delay                                                                     |                                                                                            |             | 0.6 |     | 1.0 |     | 1.2 | ns                                                                                           |
| $t_{IOE}$  | Internal output enable delay                                                                  |                                                                                            |             | 0.0 |     | 0.0 |     | 0.0 | ns                                                                                           |
| $t_{OD1}$  | Output buffer and pad delay, slow slew rate = off<br>$V_{CCIO} = 3.3\text{ V}$                | $C1 = 35\text{ pF}$<br>ocho cambia alimentazione!                                          |             | 0.8 |     | 1.3 |     | 1.8 | ns                                                                                           |
| $t_{OD2}$  | Output buffer and pad delay, slow slew rate = off<br>$V_{CCIO} = 2.5\text{ V}$                | $C1 = 35\text{ pF}$<br>abbassando aliment. => + lento                                      |             | 1.3 |     | 1.8 |     | 2.3 | ns                                                                                           |
| $t_{OD3}$  | Output buffer and pad delay, slow slew rate = on<br>$V_{CCIO} = 2.5\text{ V or }3.3\text{ V}$ | $C1 = 35\text{ pF}$<br>qui invece aggiungo                                                 |             | 5.8 |     | 6.3 |     | 6.8 | ns                                                                                           |

ovviamente i più veloci vanno a prezzi + alti (sono tutte garantite funzionanti)

|            |                                                                                                     |                      |     |     |     |     |     |      |    |
|------------|-----------------------------------------------------------------------------------------------------|----------------------|-----|-----|-----|-----|-----|------|----|
| $t_{ZX1}$  | Output buffer enable delay,<br>slow slew rate = off<br>$V_{CCIO} = 3.3 \text{ V}$                   | $C1 = 35 \text{ pF}$ |     | 4.0 |     | 4.0 |     | 5.0  | ns |
| $t_{ZX2}$  | Output buffer enable delay,<br>slow slew rate = off<br>$V_{CCIO} = 2.5 \text{ V}$                   | $C1 = 35 \text{ pF}$ |     | 4.5 |     | 4.5 |     | 5.5  | ns |
| $t_{ZX3}$  | Output buffer enable delay,<br>slow slew rate = on<br>$V_{CCIO} = 2.5 \text{ V}$ or $3.3 \text{ V}$ | $C1 = 35 \text{ pF}$ |     | 9.0 |     | 9.0 |     | 10.0 | ns |
| $t_{XZ}$   | Output buffer disable delay                                                                         | $C1 = 5 \text{ pF}$  |     | 4.0 |     | 4.0 |     | 5.0  | ns |
| $t_{SU}$   | Register setup time <small>tempo di setup per il reg.</small>                                       |                      | 1.3 |     | 2.0 |     | 2.8 |      | ns |
| $t_H$      | Register hold time                                                                                  |                      | 0.6 |     | 1.0 |     | 1.3 |      | ns |
| $t_{RD}$   | Register delay <small>tcq</small>                                                                   |                      |     | 0.7 |     | 1.2 |     | 1.5  | ns |
| $t_{COMB}$ | Combinatorial delay                                                                                 |                      |     | 0.6 |     | 1.0 |     | 1.3  | ns |
| $t_{IC}$   | Array clock delay                                                                                   |                      |     | 1.2 |     | 2.0 |     | 2.5  | ns |
| $t_{EN}$   | Register enable time                                                                                |                      |     | 0.6 |     | 1.0 |     | 1.2  | ns |
| $t_{GLOB}$ | Global control delay                                                                                |                      |     | 0.8 |     | 1.3 |     | 1.9  | ns |
| $t_{PRE}$  | Register preset time                                                                                |                      |     | 1.2 |     | 1.9 |     | 2.6  | ns |
| $t_{CLR}$  | Register clear time                                                                                 |                      |     | 1.2 |     | 1.9 |     | 2.6  | ns |
| $t_{PIA}$  | PIA delay                                                                                           | (2)                  |     | 0.9 |     | 1.5 |     | 2.1  | ns |
| $t_{LPA}$  | Low-power adder                                                                                     | (5)                  |     | 2.5 |     | 4.0 |     | 5.0  | ns |

## - MAX 3000 CPLD -

**Table 1. MAX 3000A Device Features**

| Feature               | EPM3032A | EPM3064A | EPM3128A | EPM3256A | EPM3512A |
|-----------------------|----------|----------|----------|----------|----------|
| Usable gates          | 600      | 1,250    | 2,500    | 5,000    | 10,000   |
| Macrocells            | 32       | 64       | 128      | 256      | 512      |
| Logic array blocks    | 2        | 4        | 8        | 16       | 32       |
| Maximum user I/O pins | 34       | 66       | 98       | 161      | 208      |
| $t_{PD}$ (ns)         | 4.5      | 4.5      | 5.0      | 7.5      | 7.5      |
| $t_{SU}$ (ns)         | 2.9      | 2.8      | 3.3      | 5.2      | 5.6      |
| $t_{CO1}$ (ns)        | 3.0      | 3.1      | 3.4      | 4.8      | 4.7      |
| $f_{CNT}$ (MHz)       | 227.3    | 222.2    | 192.3    | 126.6    | 116.3    |

riassumendo => avendo in input tutti i tempi mi posso calcolare (in modo automatico) tutti i tempi per i possibili percorsi => e avere così un diagramma di temporizzazioni (notare temporizzazioni indipendenti dal percorso => ovvero ad esempio il tempo di PIA è esattamente lo stesso qualsiasi sia il punto di ingresso oppure di uscita) => questo solo nel caso però di CPLD con abbastanza pochi elementi... altrimenti perdo indipendenza del percorso nel calcolo delle temporizzazioni (caso delle FPGA)



## - Examples -

per capire la frequenza massima del circuito guardo il percorso che facciamo seguendo: un registro (tcq) - il tempo di delay per il calcolo della funzione (tpia+tlad) + tempo per setup del registro (tsu) => una volta ottenuto dunque si prende il reciproco  
Evaluation of set-up, hold and Ck-to-Q time Tsuf, Thf, Tcqf at FPGA level when Tdd, Tdc, Tdq are the internal data and clock delays  
ad esempio per tempo (minimo) di 9,7 ns si ottiene una freq massima di circa 100 mega hz

$$Tsuf = Tsu + Tdd - Tdc$$

$$Thf = Th - Tdd + Tdc$$

$$Tcqf = Tdc + Tcq + Tdq$$

  

➤ For more examples see «TimingMax7000.pdf» in moodle



## - MAX 3000 CPLD -

**Table 3. MAX 3000A Maximum User I/O Pins**

| Device   | 44-Pin<br>PLCC | 44-Pin<br>TQFP | 100-Pin<br>TQFP | 144-Pin<br>TQFP | 208-Pin<br>PQFP | 256-Pin<br>FineLine<br>BGA |
|----------|----------------|----------------|-----------------|-----------------|-----------------|----------------------------|
| EPM3032A | 34             | 34             |                 |                 |                 |                            |
| EPM3064A | 34             | 34             | 66              |                 |                 |                            |
| EPM3128A |                |                | 80              | 96              |                 | 98                         |
| EPM3256A |                |                |                 | 116             | 158             | 161                        |
| EPM3512A |                |                |                 |                 | 172             | 208                        |

